

Source: [KBPhysicsMasterIndex](#)

1 | Circuits

In them, flows [KBhPHYS201Resistance](#) Resistance and Current

#disorganized

- Multiples batteries can't be solved with the combined resistor method
- So, first guess the current flow
 - Each battery's curre