

Source: [KBhPHYS201IntroToElectrostaticsLN](#)

1 | Resistance and Current

Resistance roughly measures how much pressure against current — electron flow there is in a conductor.

Current

Use the variable I , a unit $\frac{C}{s}$, *Amps*, to measure current. This also equals $\frac{\Delta V}{Resistance}$. Big resistance, little current. Current is measured in a unit $\frac{C}{s}$, which intuitively makes sense — Current/second is kind of like metres³/second — it measures, roughly, the “amount of flow”/second.

Definition 1 · **Current** I A value measured in unit $\frac{C}{s}$, a.k.a. *Amps* that measures electron flow

Resistance

So, let's figure out resistance.

We know that... $V = \frac{J}{C}$, per [KBhPHYS201Voltage](#), and we also know that resistance would equal a unit $\frac{V_s}{C}$ given that $I = \frac{C}{s} = \frac{\Delta V}{Resistance}$. Plugging in the definition of voltage, we get that resistance is measured in $\frac{Js}{C^2}$. We call this unit Ohms, or Ω .

Definition 2 · **Resistance** Ω A value measured in $\frac{Js}{C^2}$ that measures the resistance to current

Calculating resistance

- So, let's think. With a wire of length L and with a wire of area A , if we increase L , the resistance in the wire would increase; if we increase area A , the resistance in the wire would decrease.
- $Resistance = \frac{L}{A} * ResistivityOfMaterial$ with units $\frac{m}{m^2}(\Omega \times m)$.

and, indeed, resistivity of materials are measured in $\Omega \times m$, which also makes sense intuitively.

Resistors in Different configurations

Series

If you have two resistors...

--|||--|||--

With the first having a resistance of $A\Omega$ and the second $B\Omega$.

The total resistance would simply be $(A + B)\Omega$.

- Same as equivalent of “electricity!” go through the first then the second

#disorganized

Parallel

Smaller area |---||---| Bigger area |===||===|

$$R_2 = R_1 \times \frac{A_1}{A_2}$$

$$R_{eq} = R_1 \times \frac{A_1}{A_1 + A_2}$$

$$\frac{1}{R_{eq}} = \frac{A_1 + A_2}{A_1 R_1}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{A_2}{A_1 R_1}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Resistance equation for series :pointup:

#disorganized

Calculate resistance

Calculating Current in a Circuit.

Traditional Kirkob's Laws approach

A circuit!

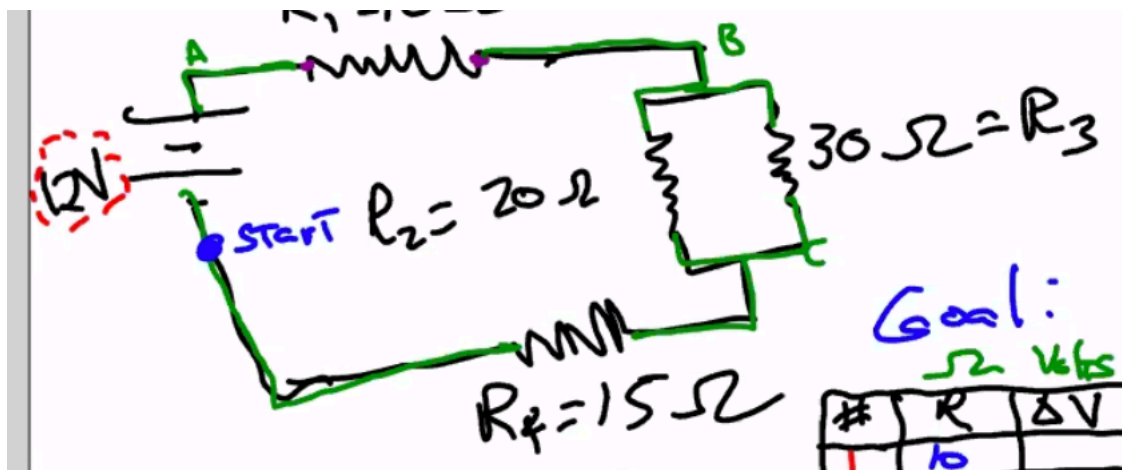


Figure 1: Screen Shot 2020-09-14 at 10.38.44 AM.png

Kirkab's First Law Sum of voltage in any closed loop should add up to 0

As in, the sum of all voltage changes from Start => Start will add up to 0.

Kirbob's Second law Net current flowing into a node is 0

With a current i_0 , when it flows into a junction like B, the current i_0 splits into i_2 and i_3

So, to calculate the resistance and current at every point o

START at start

- +12

- $-I_1 * 10$ (per $I = \frac{\Delta V}{\text{resistance}}$)
- $-I_2 * 20$
- $-I_1 * 15$
- $= 0$

$I_1 - I_2 - I_3 = 0$, per Kirerbab's Second Law.

Through a resistor, the Current does NOT change, the Voltage drops.

"Combine Resistors" Method

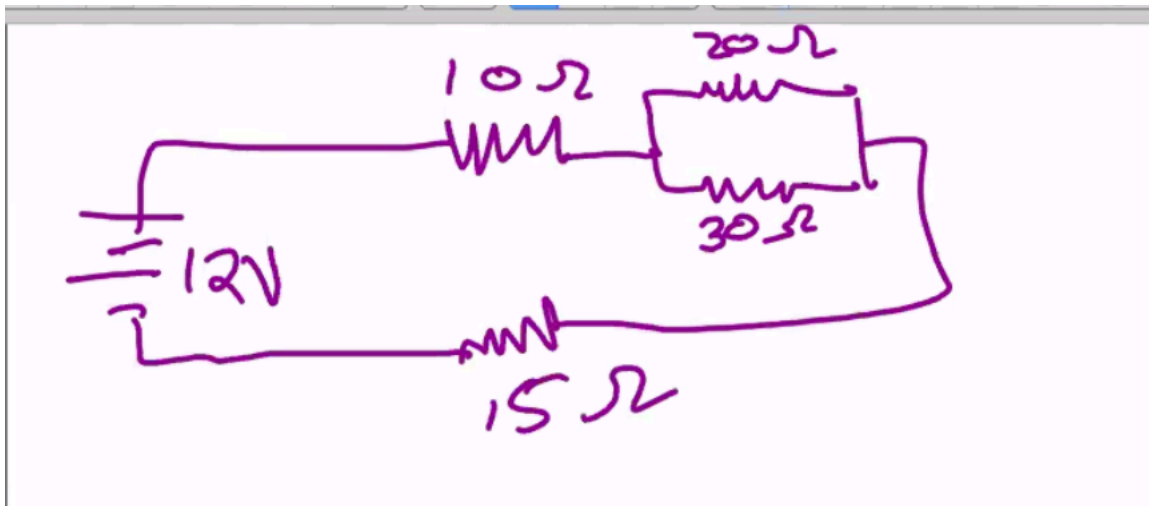


Figure 2: Screen Shot 2020-09-14 at 11.02.45 AM.png

Parallel Resistors as Single Resistors Per the previous resistors rules