

Source: [KBhPHYS201CircuitCalculations](#)

1 | Combining Resistors Method

The [KBhPHYS201KirkoffsLaws](#) Kirkoff's Laws themselves often requiring solving >6x6 matrixes to solve equations quickly. Which is hard.

Series

If you have two resistors...

--|||--|||--

With the first having a resistance of $A\Omega$ and the second $B\Omega$.

The total resistance would simply be $(A + B)\Omega$.

- Same as equivalent of "electricity!" go through the first then the second

#disorganized

Parallel

Smaller area |--|||-- | Bigger area |===|||===

$$R_2 = R_1 \times \frac{A_1}{A_2}$$

$$R_{eq} = R_1 \times \frac{A_1}{A_1 + A_2}$$

$$\frac{1}{R_{eq}} = \frac{A_1 + A_2}{A_1 R_1}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{A_2}{A_1 R_1}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Resistance equation for series :pointup:

#disorganized

Calculate resistance

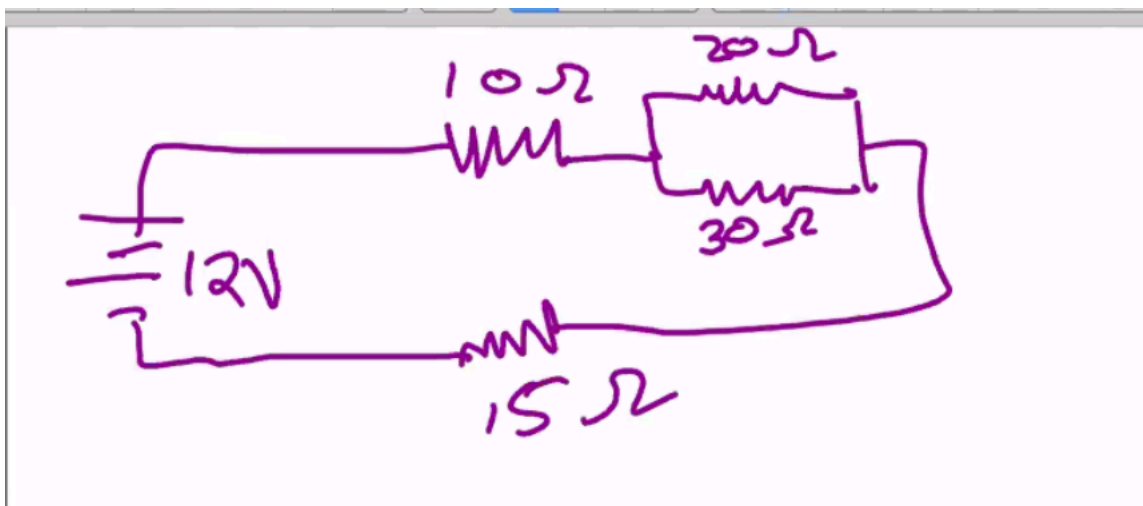
“Combine Resistors” Method

Figure 1: Screen Shot 2020-09-14 at 11.02.45 AM.png

Parallel Resistors as Single Resistors Per the previous resistors rules, that $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$, we could treat the 20Ω and 30Ω in parallel as a single resistor of 12Ω.

Now the circuit becomes even simpler:

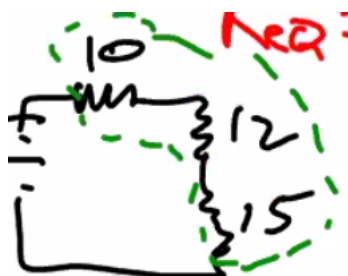


Figure 2: Screen Shot 2020-09-14 at 11.05.49 AM.png

Sequence Resistors as Single Resistors Per the sequence resistors rules, that total resistance is $(A + B)\Omega$, we could combine these three resistors as a 37Ω resistor.

Combined Current We know that $12V/37\Omega = 0.324Amps$ is the current that returns to the battery and what the battery starts with, for if we treat the circuit as a single resistor, the 12 volts would only be working against.

From there, once we have a current for beginning and end, we could work our way up backwards by calculating the final voltage.

- Multiples batteries can't be solved with the combined resistor method
- So, first guess the current flow
 - Each batteries' current will flow back to itself
 - When currents meet, they will combine

- Use currents identified before + Kirkoff's second law
- Use Kirkoff's first law to find loops (and hence equations) that, together, **covers all components**
- If resulting currents is negative, that means that you drew the current in the wrong direction, or you are charging a battery
 - Either way, if the signs are preserved to solve the rest of the equation, you should be fine numerically
 - Just update your graph to reflect the actual currents' directions

LED longer leg is positive