

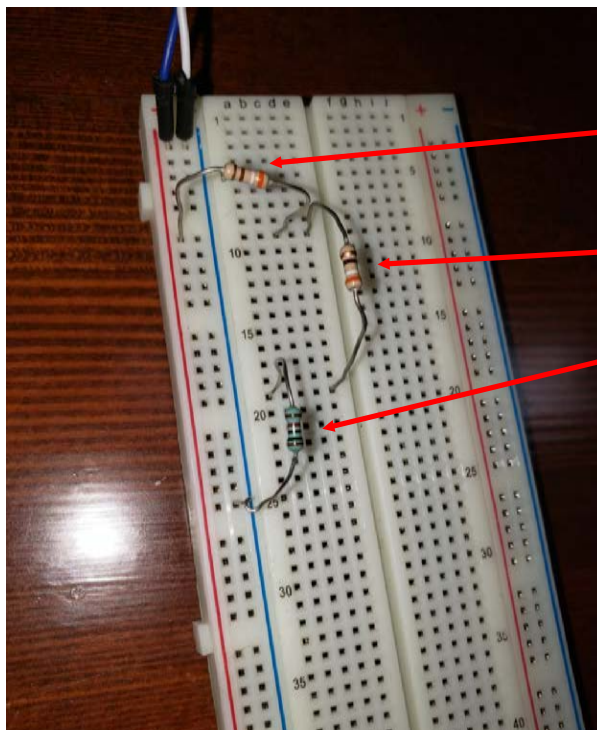
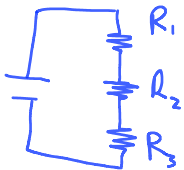
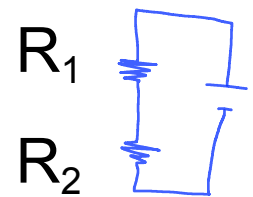


Assume that the + and - rails are correctly connected to the corresponding ends of a 3V battery pack. Draw a circuit diagram corresponding to each image. Comment on anything that seems incorrect or unusual about each circuit. Label each resistor  $R_1$ , etc. as shown - no need to read quantitative resistances from the color bands.

 $R_1$  $R_2$  $R_3$

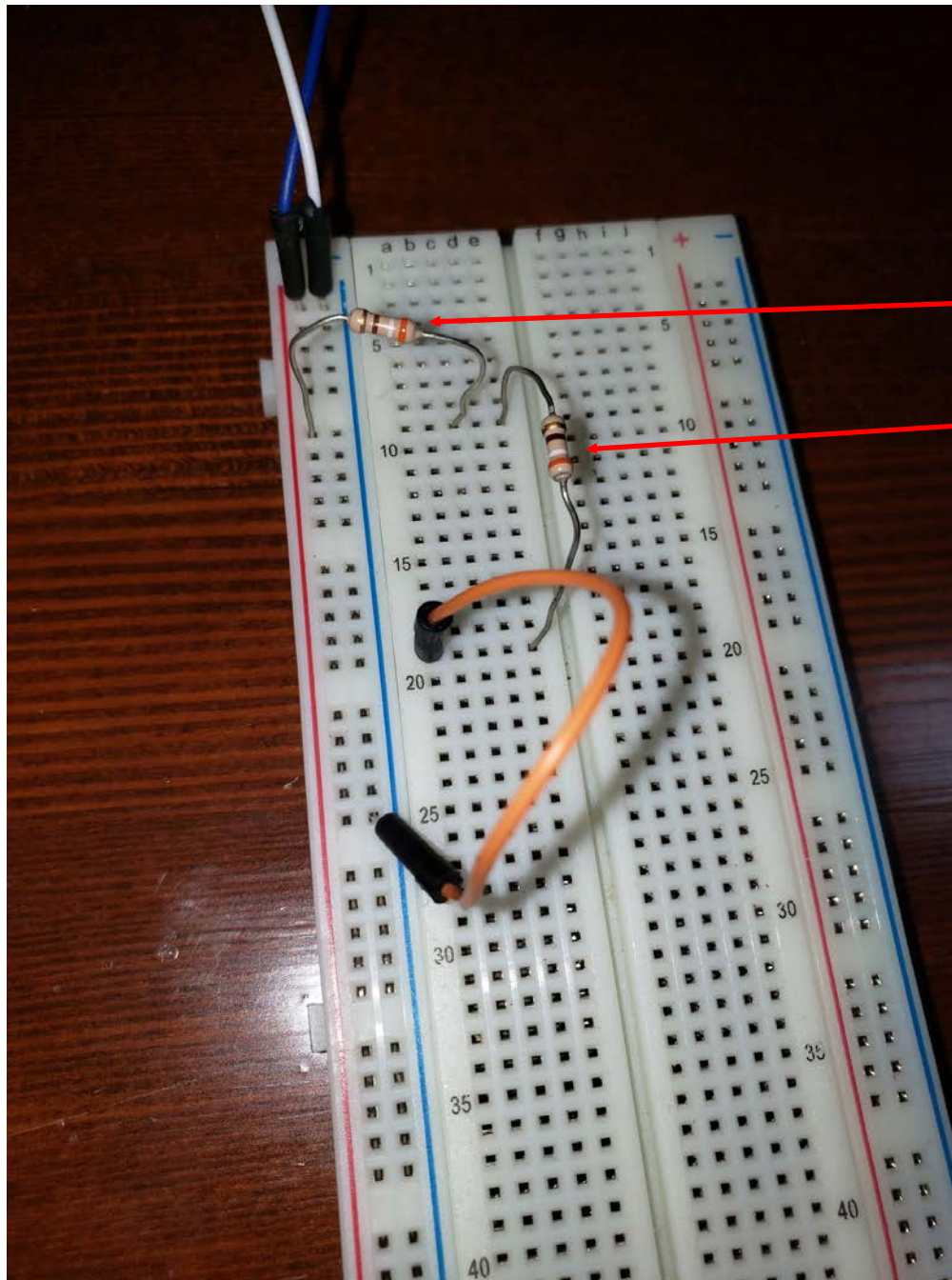

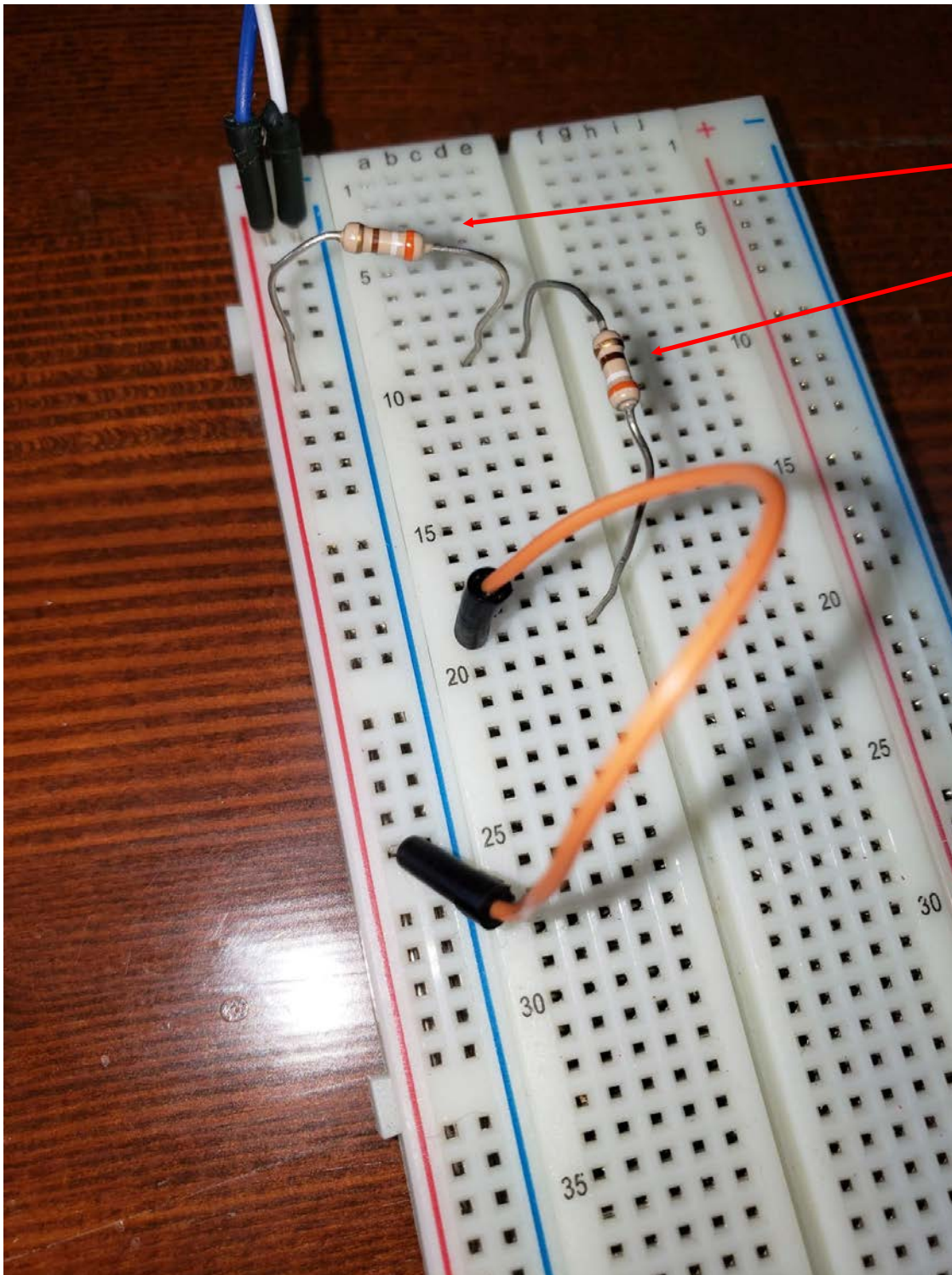


$R_1$

$R_2$






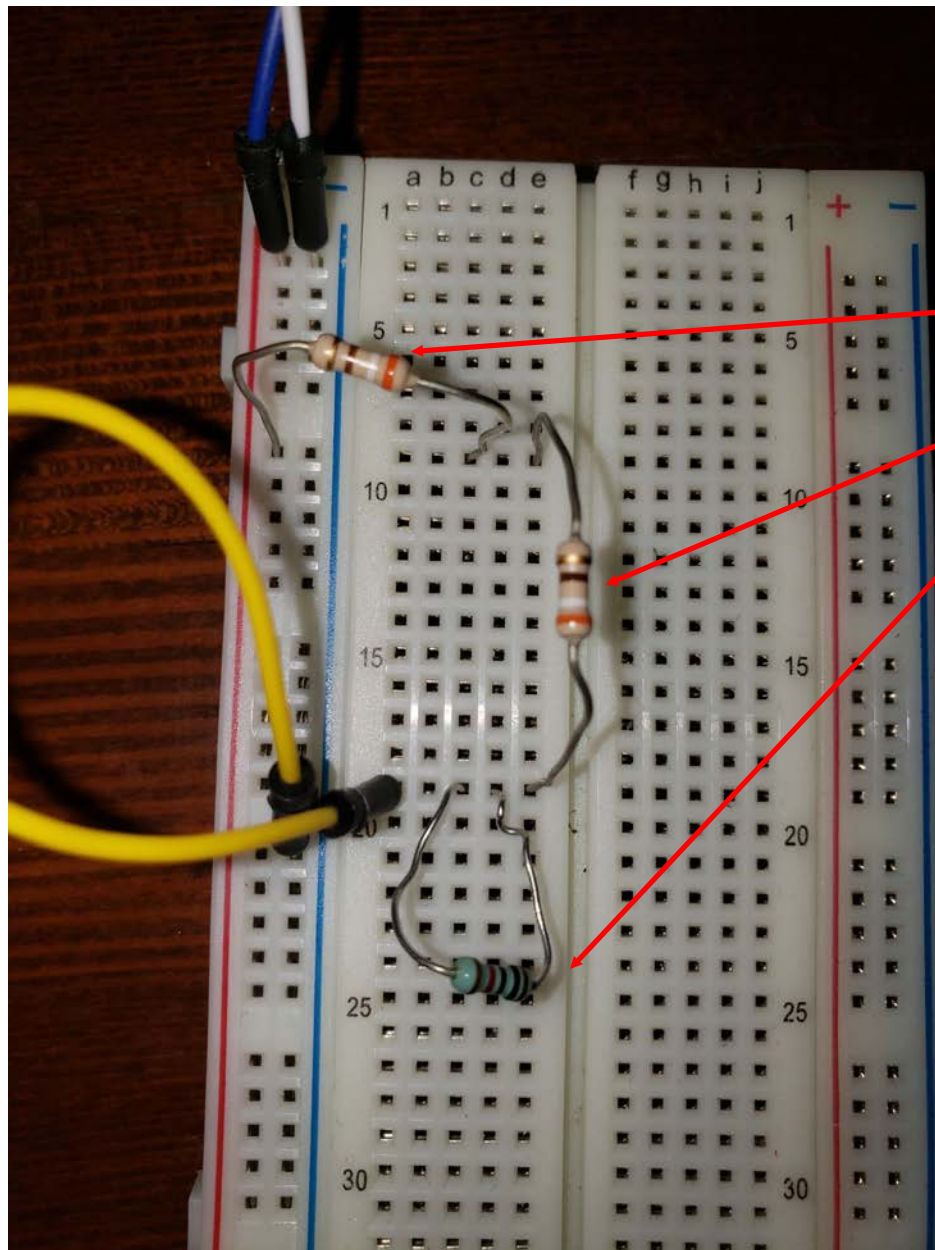



$R_1$

$R_2$


$R_3$

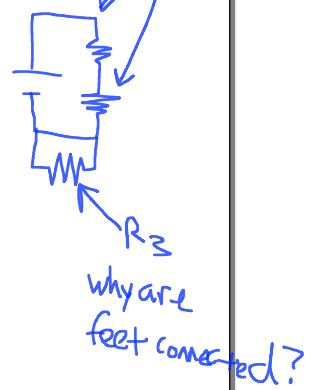

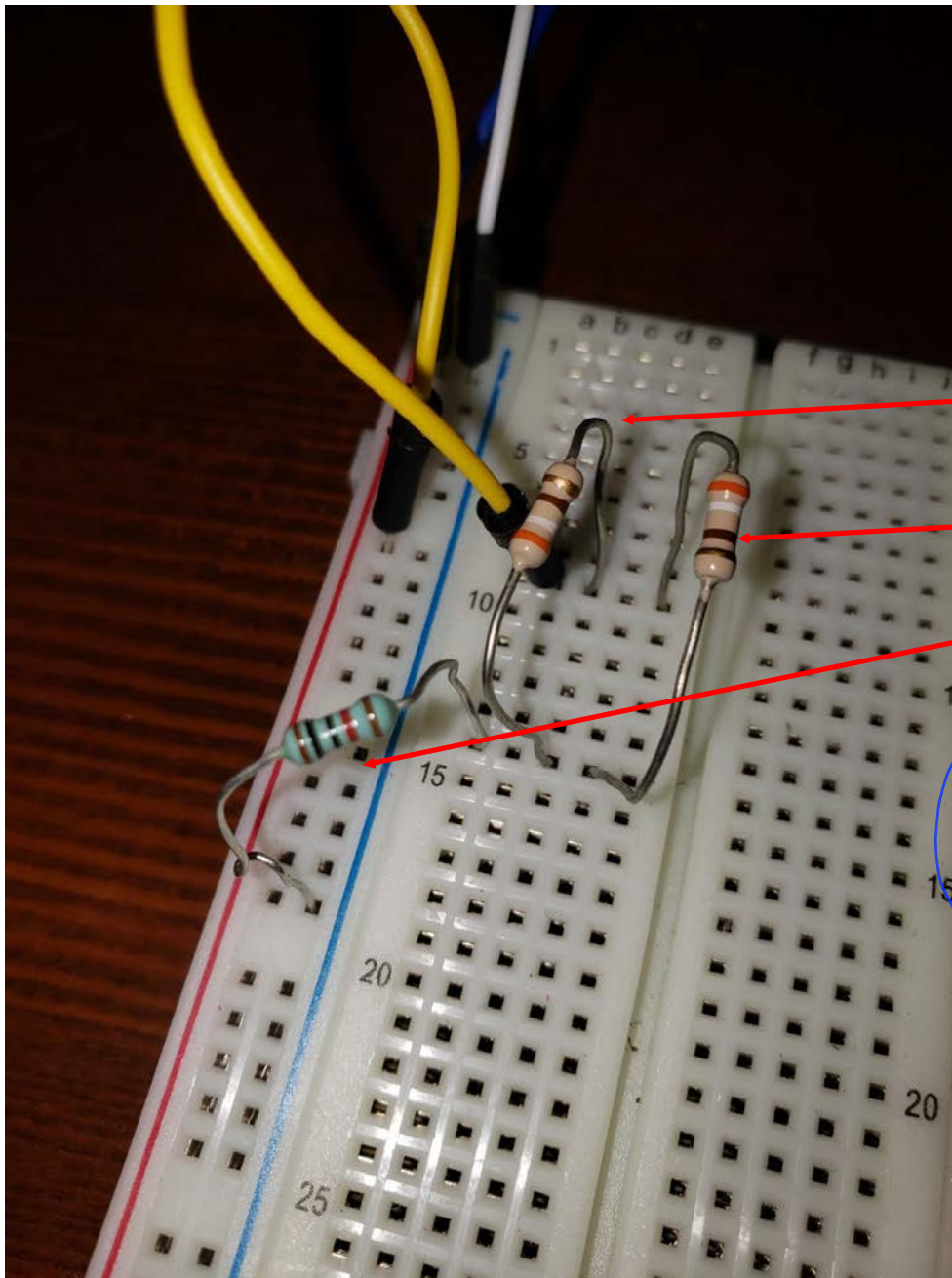

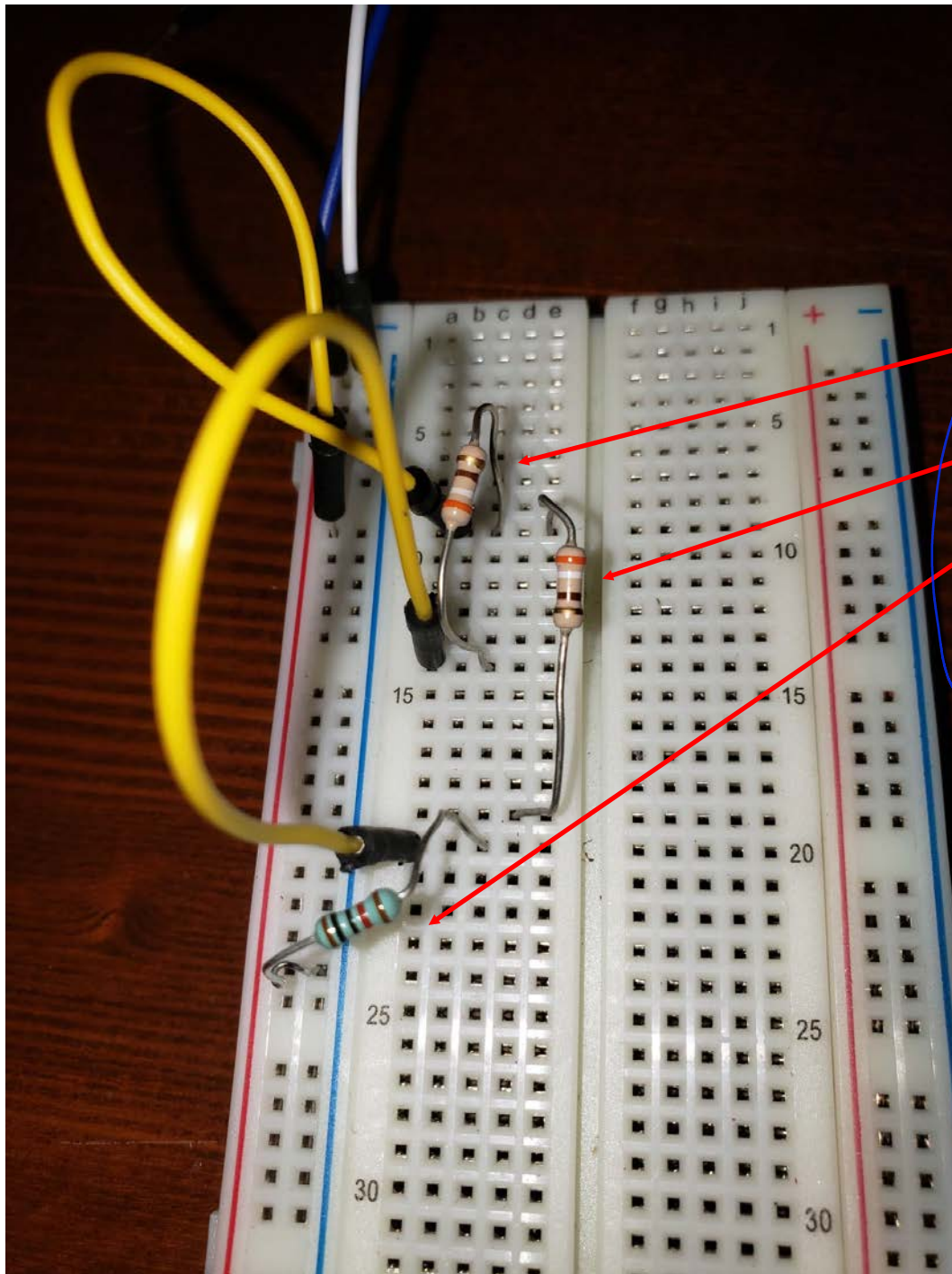




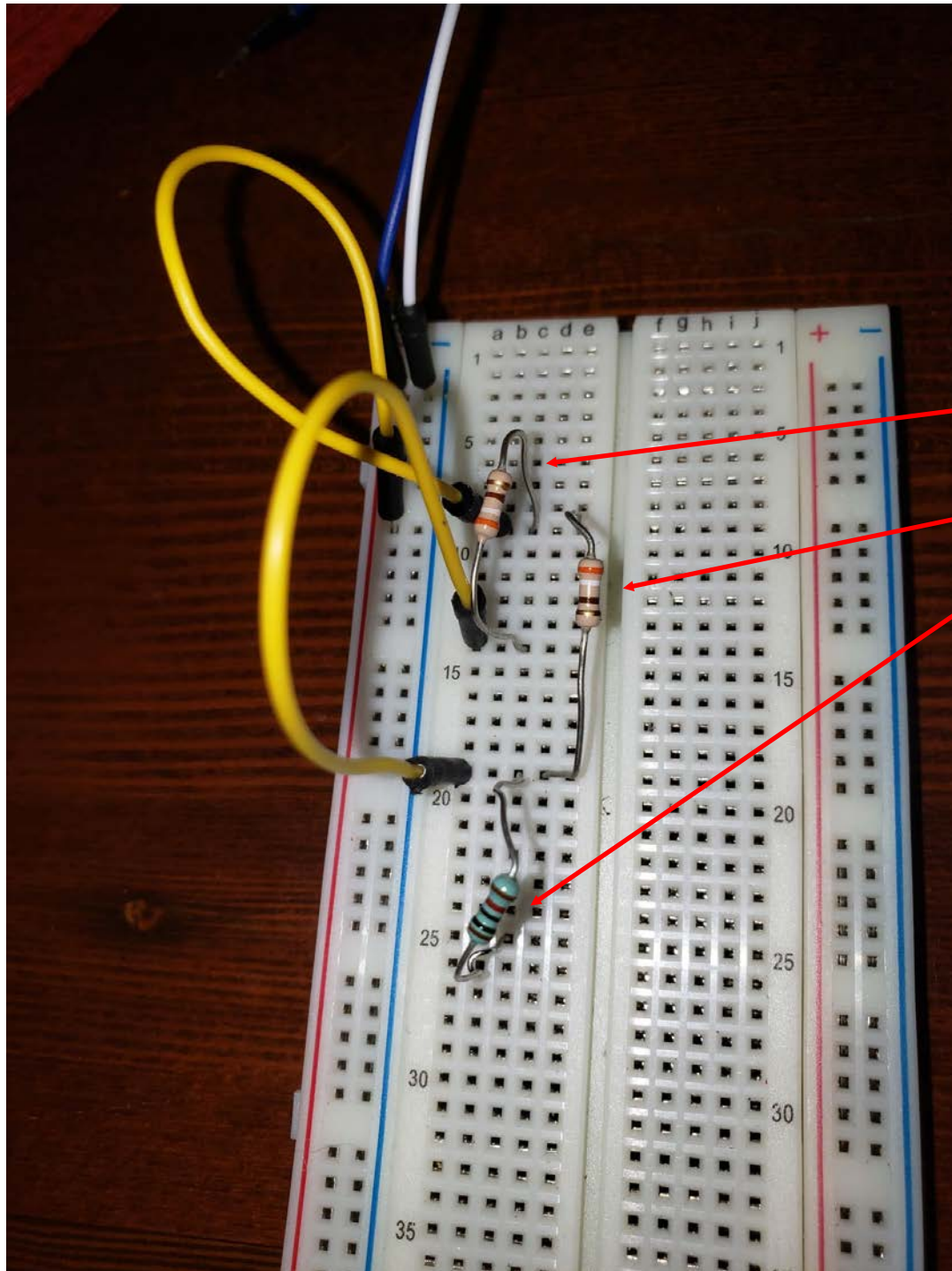


$R_1$

$R_2$

$R_3$

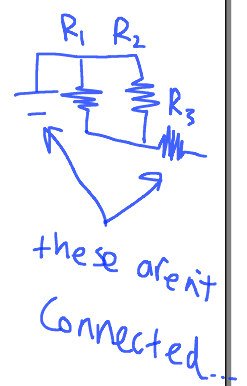


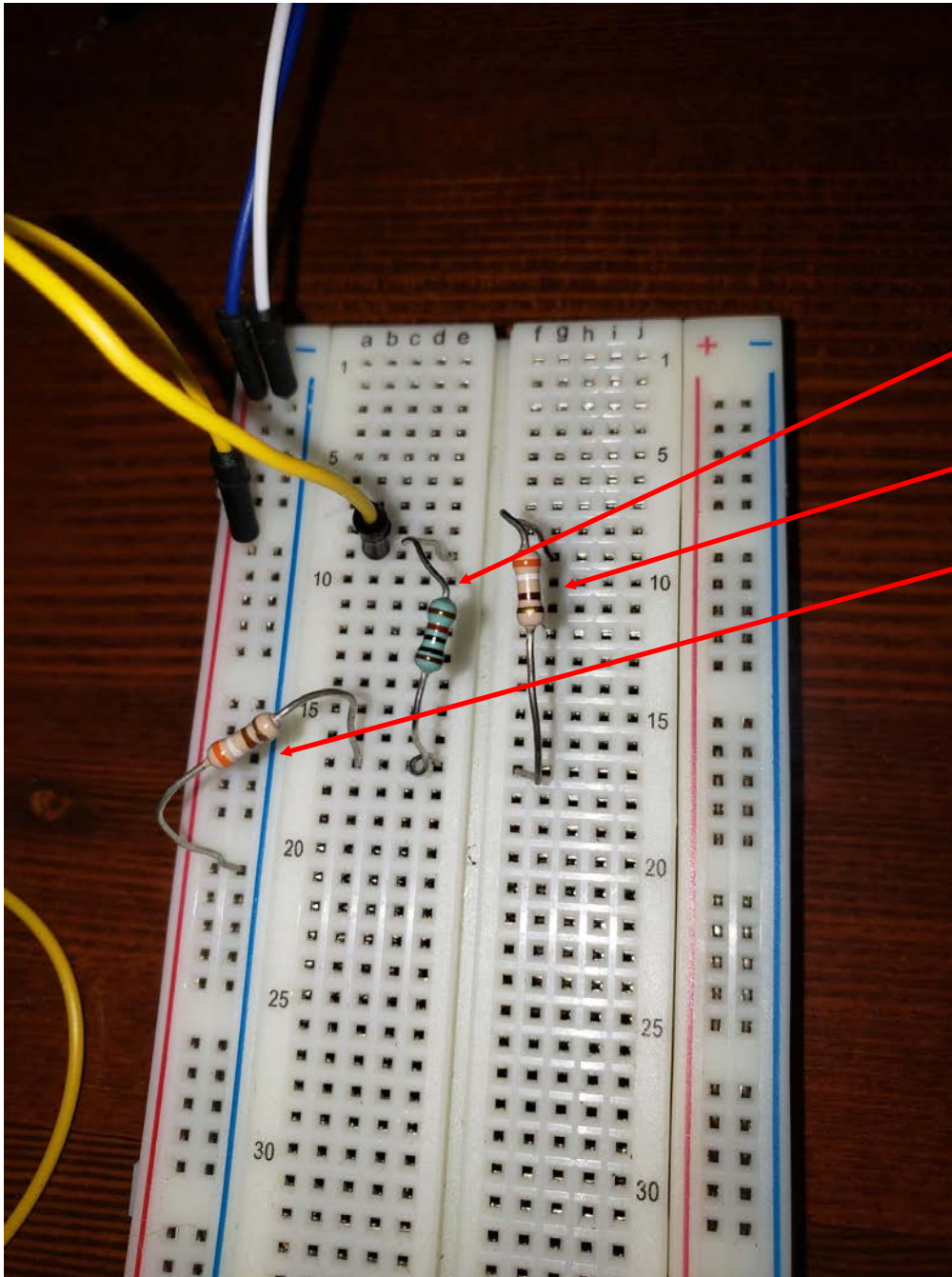


$R_1$

$R_2$

$R_3$

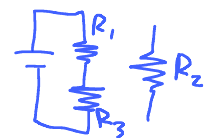



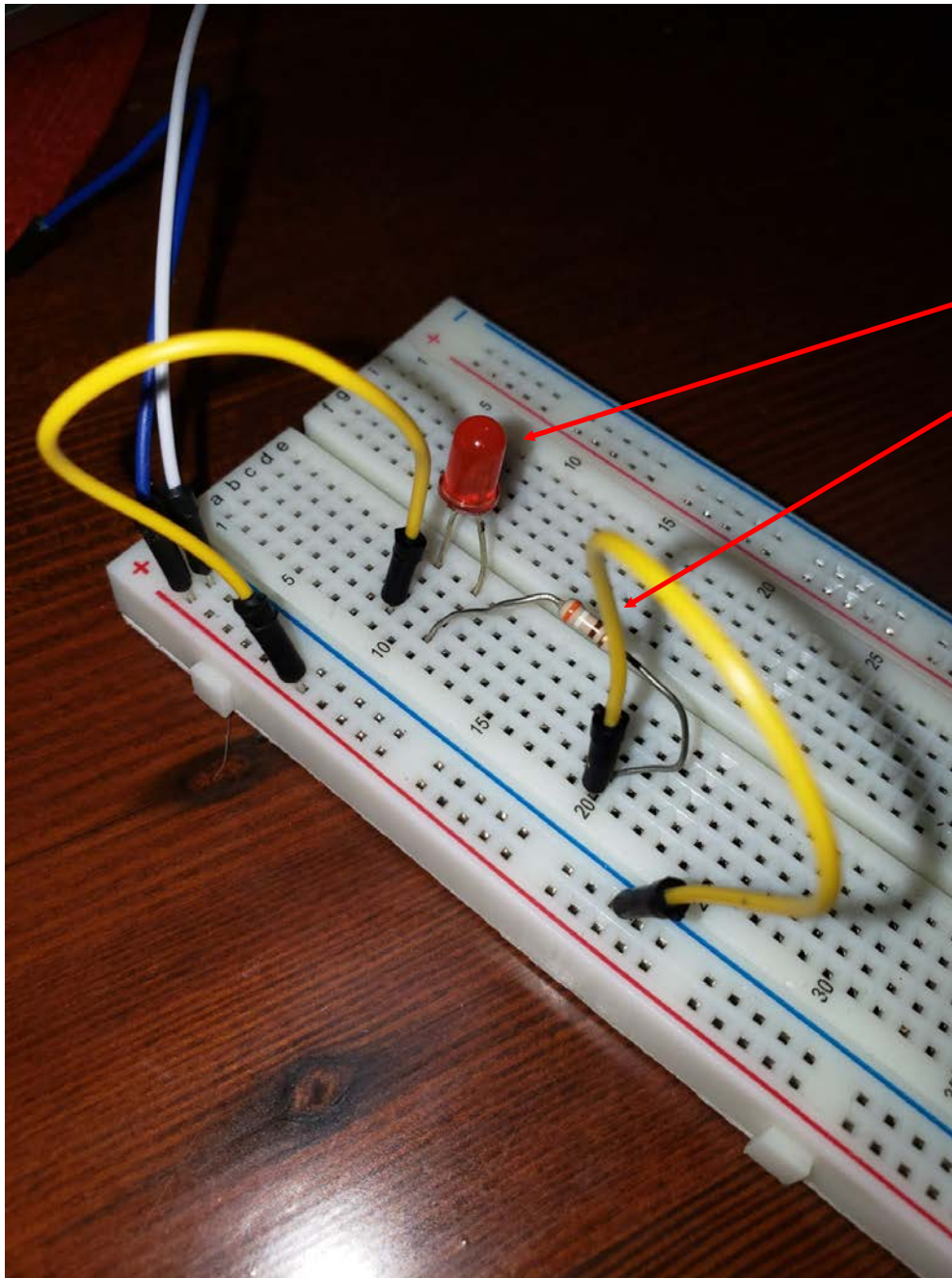


LED

R<sub>1</sub>

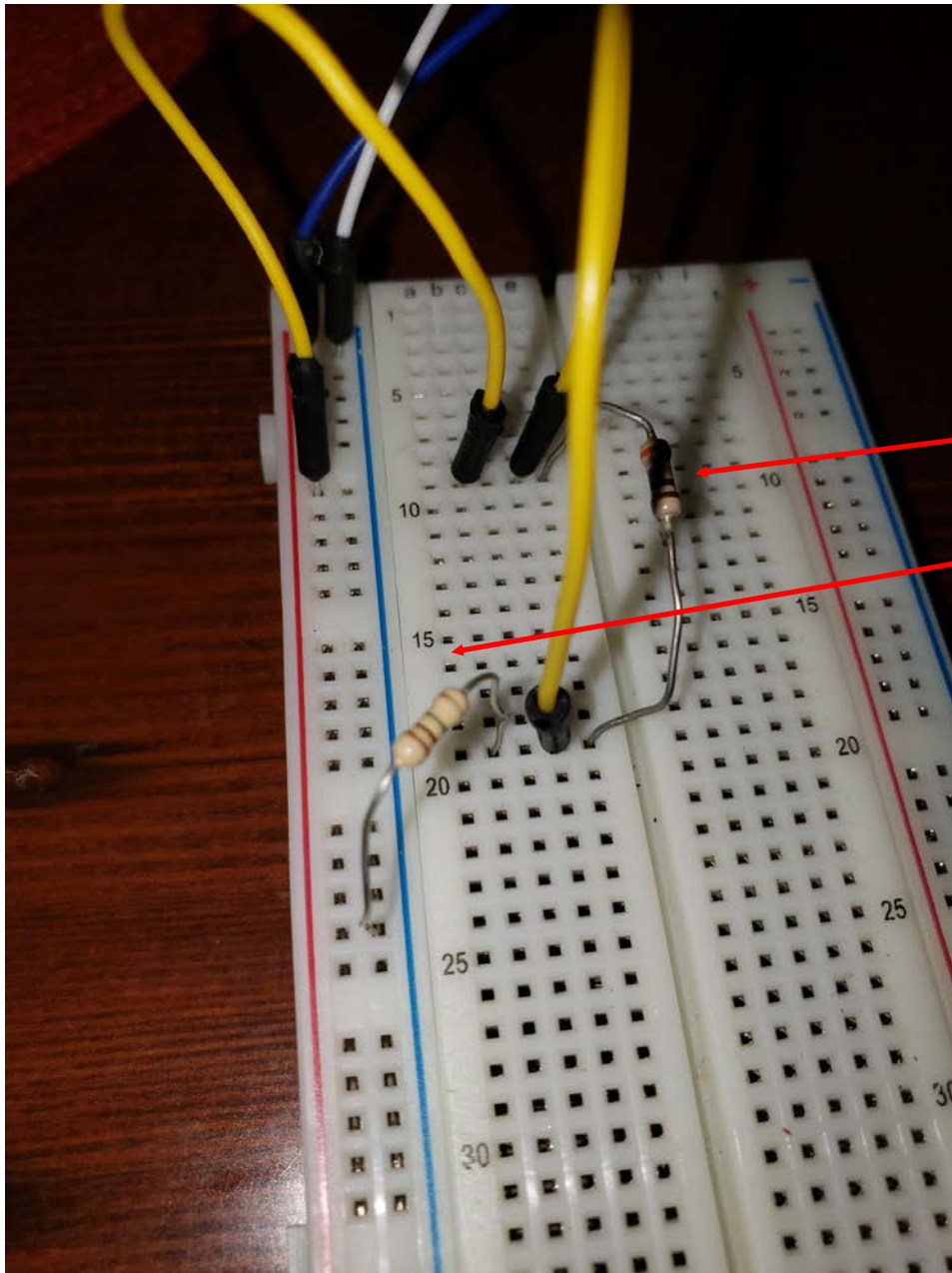I can't see the inside of the LED, so I can only assume that the bottom right leg is the positive. I think it's going in the wrong direction..





$R_1$

$R_2$

doesn't do much

